

Last Lecture :-

- Basic arithmetic circuit design

- Half adder (to add two single bit)
- Full adder (to add three single bit)
- n-bit ripple carry adder
- Adder Subtractor (to ~~add~~ two n-bit numbers)
- (to add or subtract two n-bit number)

- Today's Lecture :-

- Multiplier Design
- ALU Design

Multiplier Design :-

Two bit Multiplication :-

b ₁	a ₁	mul
0	0	0
0	1	0
1	0	0
1	1	1



AND operation



② Multiplication of two ^{n-bit} numbers

Lets try for 4-bit number:-

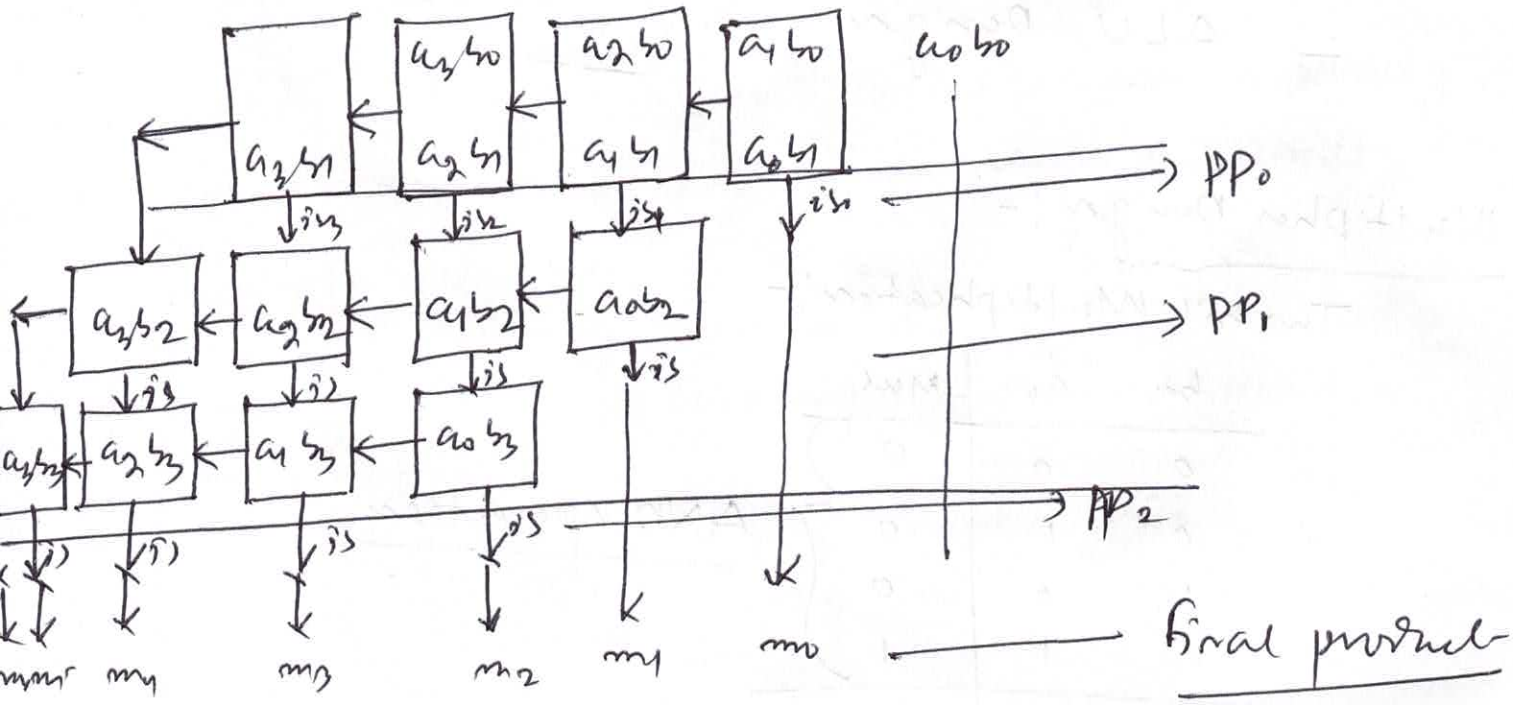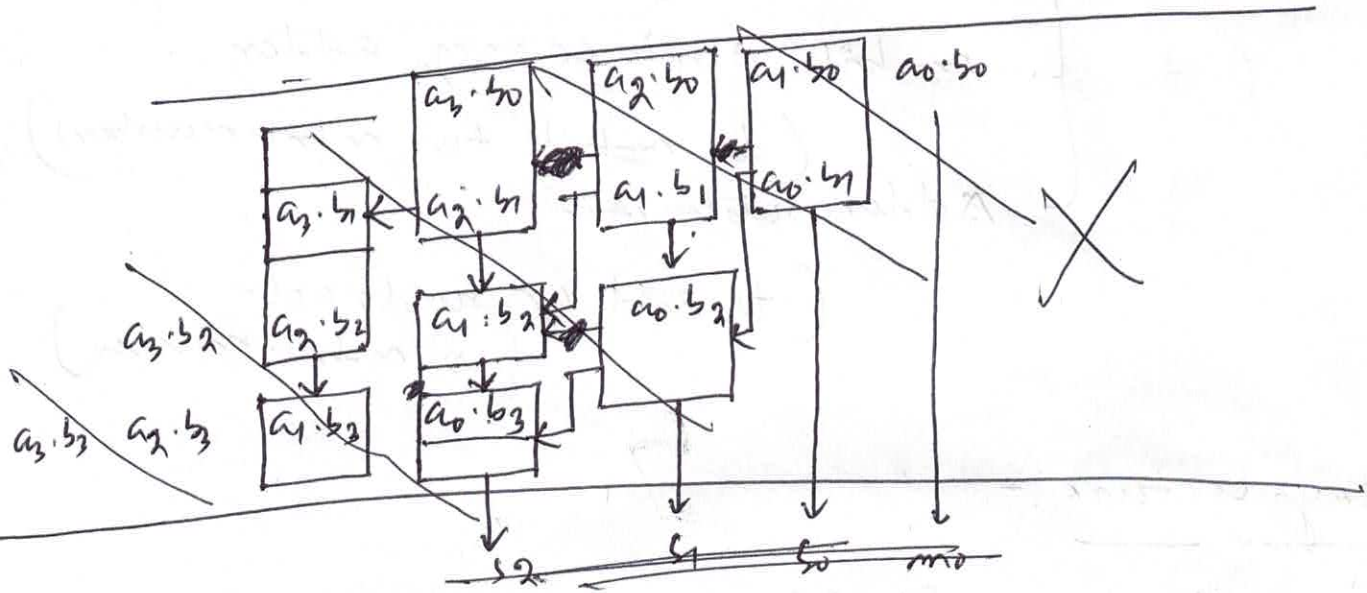$a_3 \quad a_2 \quad a_1 \quad a_0$
 $b_3 \quad b_2 \quad b_1 \quad b_0$




Basic Hw for Multiplier

→ Reuse the ripple carry adder layer by layer

ALU Design :-

~~Easy & inefficient way :-~~

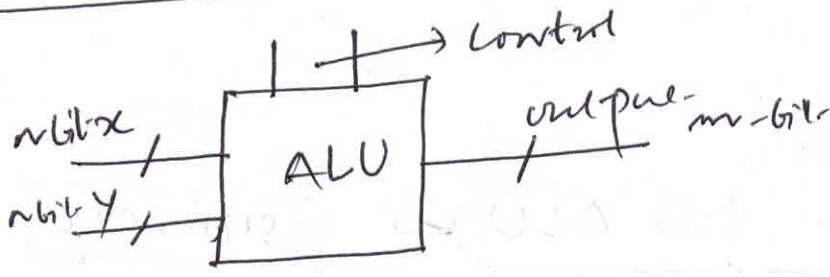


Easy & inefficient way of design :-

The required functionality -

- Addition $(x+y)$
- Subtraction $(x-y)$
- Logical AND $(x \wedge y)$
- Logical OR $(x \vee y)$

Circuit Design :-

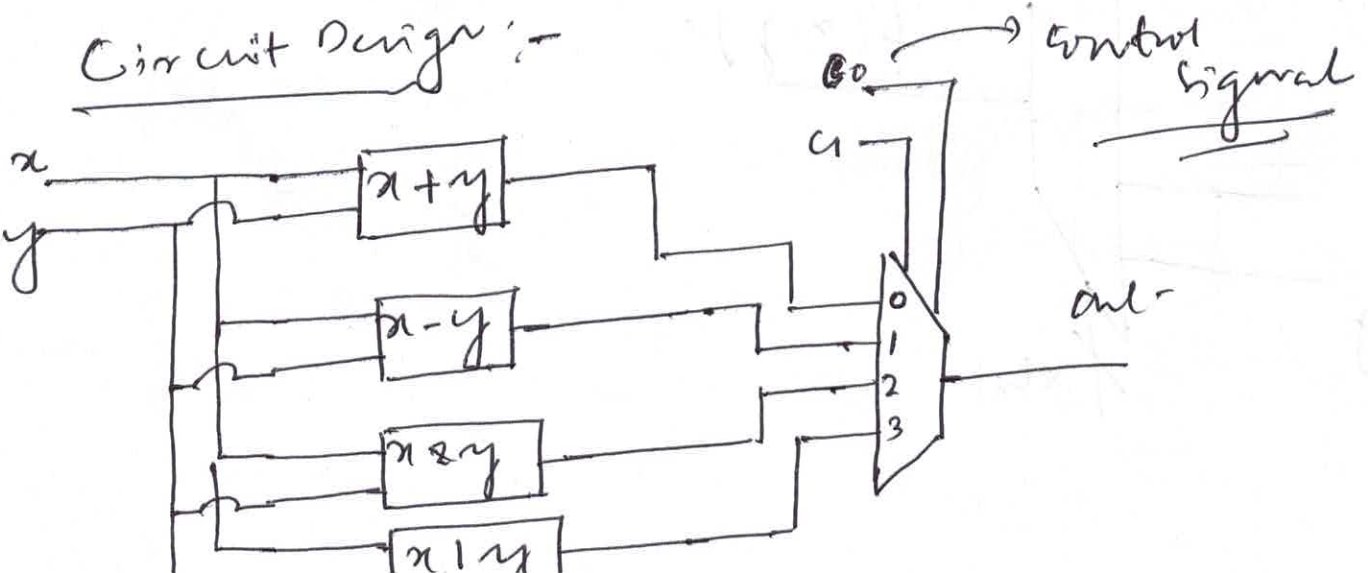

4

Control signal


C_1	C_0	$f(x, y)$
0	0	ADD
0	1	SUB
1	0	AND
1	1	OR

~~Design~~

Design of 16-bit ALU in CS410 ALU


Specification :- 16 bit, two inputs
16 bit one output

Easy and in-efficient way of design :-

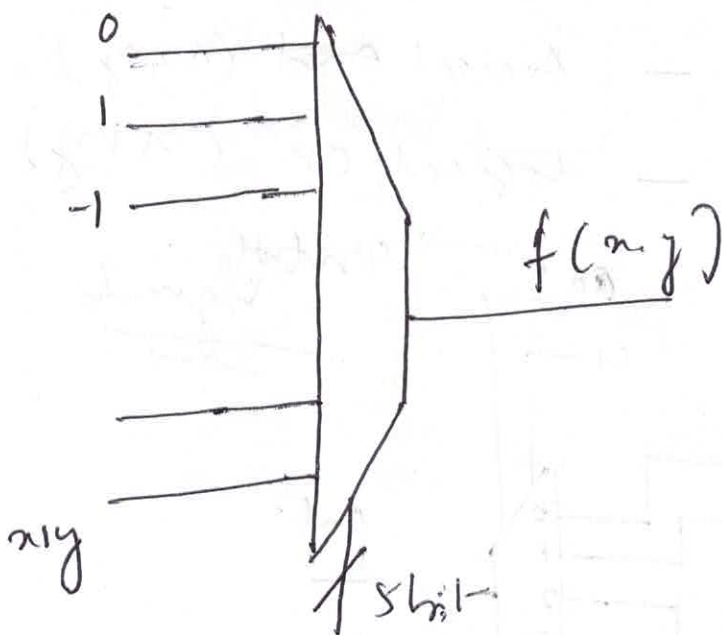

Sufficient- ALU Design :

Size - 16 bit & 32 bit
ALU16 | ALU32

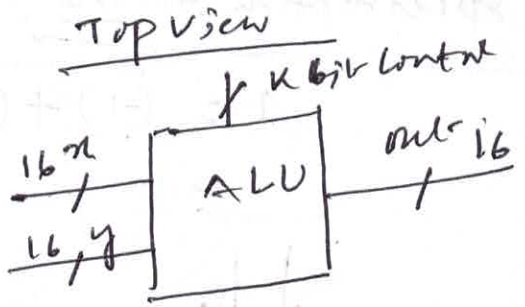

Functionality :-


- 0 =
- 1 =
- 1 =
- x =
- y =
- \bar{x} =
- \bar{y} =
- x =
- y =
- x+1 =
- y+1 =
- x-1 =
- y-1 =
- x+y =
- x-y =
- y-x =
- x&y =
- x|y =
- $\overline{x&y}$ =
- $\overline{x|y}$ =

Design principles :-

- ① Find out the compulsory unit.
- ② Derive remaining ~~functionality~~ functionality around ~~the~~ the compulsory unit.


Compulsory Unit :-

⊕ Adder :- x+y

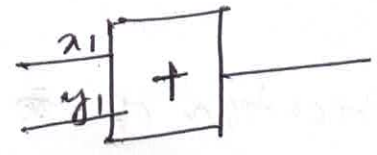

Specification for zero :-

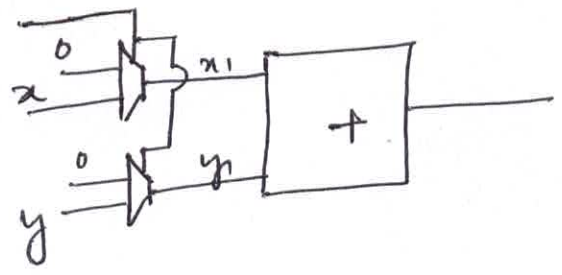
Irrespective of any value in x & y the output should be zero.



6

Specification for one :-
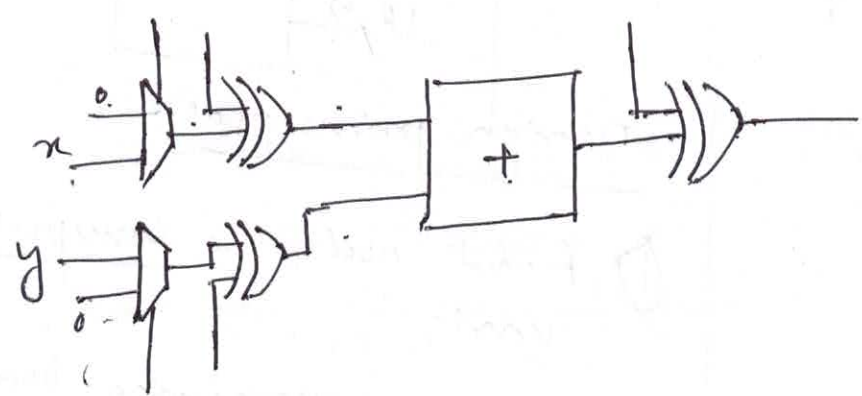
$$1 = (-1) + (0) = (-2) = (110) = 001 \checkmark$$



Specification for -1 :-

$$\boxed{-1 + 0 = -1}$$


Irrespective of any input of x or y the output should be -1.

Specification of x :-

Irrespective of any input input the output should always be x.

$$\rightarrow x + 0$$
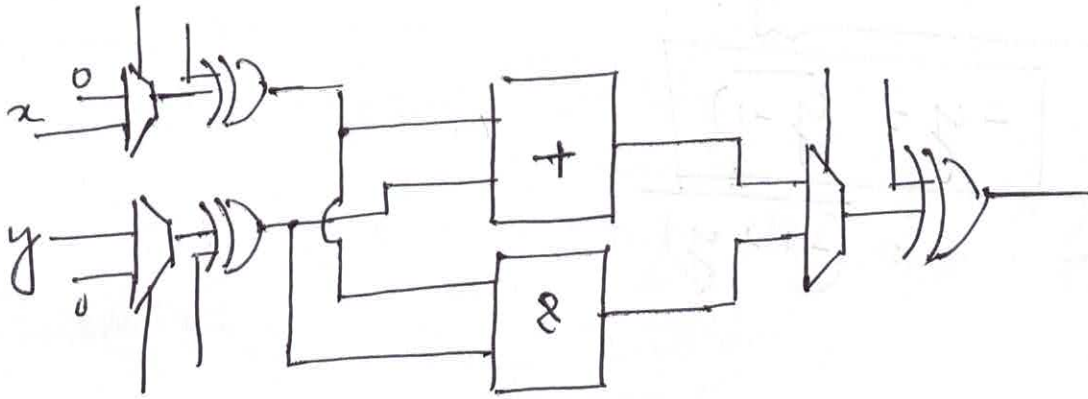
$$\begin{aligned} \rightarrow x \&(-1) &= x \&(1111\dots 1) = x \\ &= x \&(0000\dots 0) \\ &= x \&\underline{\underline{0}} \end{aligned}$$



Specification for y :-

Always 'y' irrespective of x

$$\rightarrow y \oplus 0 = y$$

$$\rightarrow (-1) \& y = y$$

Specification for \bar{x} :-

$$\rightarrow \bar{x} = \overline{x \& (-1)}$$

$$\rightarrow \bar{x} = \overline{(x + 0)}$$

Specification for \bar{y} :-

$$\rightarrow \bar{y} = \overline{(-1) \& y}$$

$$\rightarrow \bar{y} = \overline{(0 + y)}$$

Specification for $-x$:-

$$-x = \bar{x} + 1$$

$$\Rightarrow -x - 1 = \bar{x}$$

$$\Rightarrow -(x - 1 + 1) = \overline{(x - 1)} \quad (\text{let } x = x - 1)$$

$$\Rightarrow -x = \overline{(x - 1)}$$

⑧ Specification for $-y$:-

$$\boxed{-y = \overline{(y-1)}} \\ = \overline{(-1+y)}$$

Specification for $(x+1)$:-

$$-x = \bar{x} + 1 = \overline{(x-1)}$$

$$\Rightarrow y+1 = \overline{(y-1)} \quad (\text{let } \bar{x} = y)$$

$$\Rightarrow x+1 = \overline{(x-1)} \quad (\text{let } x = y) \\ = \overline{x+(-1)}$$

Specification for $(y+1)$:-

$$\boxed{y+1 = \overline{(-1)+y}}$$

Specification for $(x-1)$:-

$$\boxed{x-1 = x+(-1)}$$

Specification for $(y-1)$:-

$$\boxed{y-1 = (-1)+y}$$

Specification for $(x+y)$:-

$$\boxed{x+y = x+y}$$

$$\Rightarrow m = x+y, \text{ but } \underline{x=x \wedge y=y}$$

Specification

Specification for $(x-y)$:-

$$\boxed{m = x-y}$$

$$\text{but } \begin{matrix} x = x \wedge \\ y = y \end{matrix}$$

$$-x = \bar{x} + 1$$

$$\Rightarrow -x - 1 = \bar{x}$$

$$\Rightarrow -x + y - 1 = \bar{x} + y$$

$$\Rightarrow -(x-y) - 1 = \bar{x} + y$$

$$\Rightarrow -z - 1 = \bar{x} + y$$

$$\Rightarrow \bar{z} = \bar{x} + y$$

$$\Rightarrow \overline{x-y} = \bar{x} + y$$

$$\Rightarrow \boxed{x-y = \overline{\bar{x} + y}}$$

$$(let\ x = y = z)$$

$$(\overline{let\ z = x - y})$$

Specification for $(y-x)$:-

$$y-x = \overline{\bar{y} + x}$$

$$\boxed{y-x = \overline{x + \bar{y}}}$$

Specification for $(x \& y)$:-

$$\boxed{\text{out} = x \& y}$$
 when $x = a$ and $y = b$

Specification for $(x | y)$:-

$$\text{out} = x | y \quad (\text{OR operation})$$

$$x | y = \bar{x} \& \bar{y}$$

Exercise :-

Find out the control signal for following :-

- (B1) NAND $\rightarrow \overline{x \& y} \rightarrow \text{Easy}$
- (e2) NOR $\rightarrow \overline{x | y} \rightarrow \text{Easy}$
- (e3) XOR $\rightarrow x \oplus y \rightarrow \text{Moderate difficulty}$
- (e4) XNOR $\rightarrow \overline{x \oplus y} \rightarrow \text{Moderate difficulty}$

~~(e5)~~ \rightarrow $\boxed{\text{Multiplication} \rightarrow x * y}$

(e5) Comparator :- \hookrightarrow This will require additional functional unit and a control signal.

- less than $x < y$
- equal $x = y$
- greater $x > y$

(e6)